


Week	Activity	Resources	How presented?
1	<p>Task 1 Quantum physics Watch the video https://www.youtube.com/watch?v=zBTbqOgdfEY Make sure you can answer these questions by the end of it (make some notes or flashcards):</p> <ol style="list-style-type: none"> 1. What did Planck discover? 2. How did Einstein explain the photoelectric effect? 3. How did Bohr explain an atoms stability? <p>Open the simulation below and explore how it links to the video and the photoelectric effect https://phet.colorado.edu/en/simulation/legacy/photoelectric</p> <p>Research one or more of the following topics related to quantum physics (make some notes or flashcards):</p> <ol style="list-style-type: none"> 1. Absorption and emission spectra 2. Electron diffraction 3. Schrödinger's cat 4. Heisenberg uncertainty principle <p>Task 2 Electric circuits Complete the worksheet Current Voltage and resistance (below) using the equation p.d. = current x resistance ($V=IR$) and the circuit rules explained in these videos</p> <p>GCSE Science Revision Physics "Current in Parallel Circuits" - YouTube</p> <p>GCSE Science Revision Physics "Potential Difference in Parallel Circuits" - YouTube</p> <p>then construct the circuits using this app: https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc_en.html and test to see if your calculations are correct.</p> <p>Include a photo of your answers and include them on the Powerpoint</p>	Web site as listed	<p>Record your work on Powerpoint or Word. You will then add further tasks into this document over the next 3 weeks (which you will then send to your A – level teachers)</p> <p>Include a photo of your answers and include them on the Powerpoint</p>

Current, Voltage and Resistance


Apply the rules of current and voltage to the following circuits and use the $V=IR$ equation to work out the missing currents, voltages and resistances as required. Unless stated otherwise, assume all bulbs are identical. **DON'T FORGET YOUR UNITS!**

Remember: To work out resistors in series $R_{Total} = R_1 + R_2 + R_3$

1.

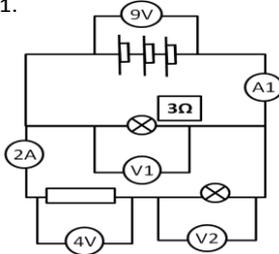


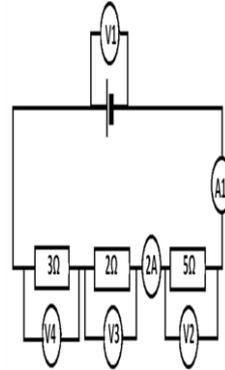A1 = _____
 A2 = _____
 V1 = _____
 V2 = _____
 V3 = _____




A1 = _____
 A2 = _____
 A3 = _____
 V1 = _____
 V2 = _____
 V3 = _____
 R1 = _____

2.

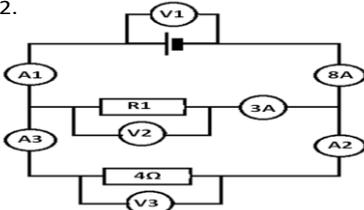


A1 = _____
 A2 = _____
 V1 = _____
 R1 = _____

6.

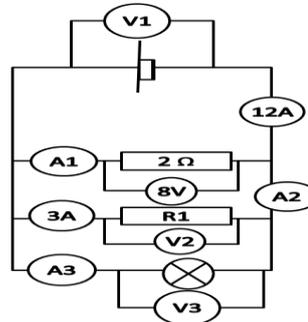


A1 = _____
 A2 = _____
 A3 = _____
 V1 = _____
 V2 = _____
 R1 = _____
 R2 = _____

3.

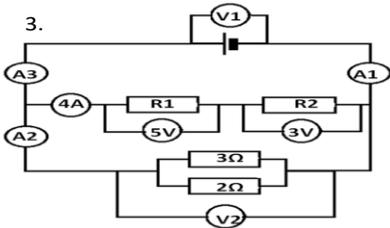


A1 = _____
 V1 = _____
 V2 = _____
 V3 = _____
 V4 = _____

4.

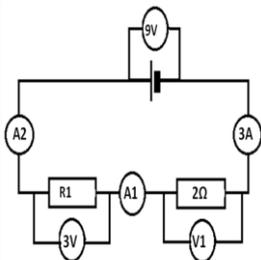

A1 = _____
 V1 = _____
 V2 = _____
 Calculate the resistance of:
 The bulb = _____
 The resistor = _____

7.

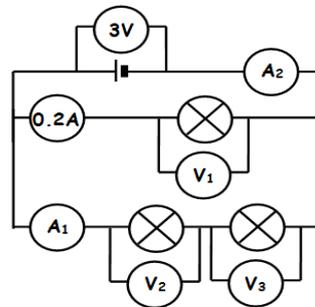

A1 = _____
 A2 = _____
 A3 = _____
 V1 = _____
 V2 = _____
 V3 = _____
 R1 = _____